


2024/2025

## EXAM S3 : Electrotechnique fondamentale 1
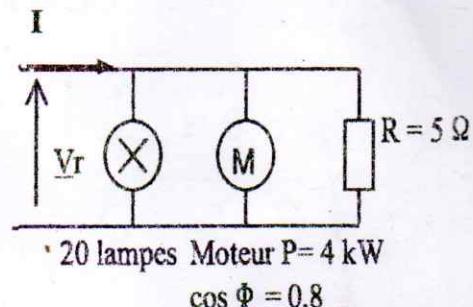
### EX:01 : (6Pts)

The power of a single lamp is 260W and  $V_r=110V$

- What are the active and reactive powers consumed by the installation?
- What is the power factor?
- What is the effective intensity of the current ( $I$ ) in the line cable?



### EXE 01 : (8Pts)

Consider the following circuit, the current intensity is 2 A, the relative permeability of the material is  $\mu_r=2500$  with an air gap thickness of 0.5 cm, the number of turns is 250. Knowing that the depth is 4 cm, calculate:


- Calculate the reluctance of this circuit (material and air gap) and calculate the magnetic flux? Give the equivalent electrical diagram?

- Indicated what this information corresponds to, taken from the nameplates of two transformers: Yy6 and Dy5
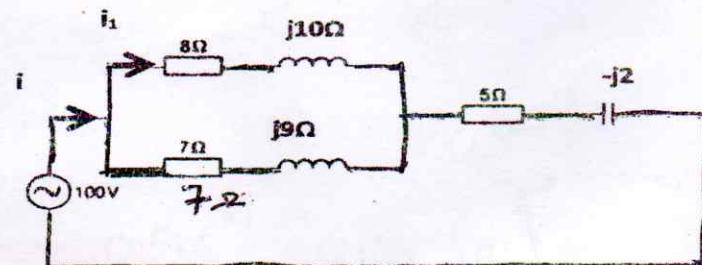
### EXE 03 : (6Pts)

We consider the circuit represented in the figure 03 . Knowing that  $V(t)=220\sqrt{2}\sin 314t$ .

- Calculate the impedances of each branch
- Calculate the equivalent impedance ( $Z_{eq}$ ) and the current i(t),
- What is the nature of the charge



DG handelbaren System:

ELTF: 01

$S_3$

EXO 1 (6 pts)

a) Lampe:  $2600 \text{ W}$

$$P_{\text{Lampe}} = 20 \times 2600 = 5,2 \text{ kW}$$

$$P_H = 4 \text{ kW}$$

$$P_L = 5,2 \text{ kW}$$

$$P_R = 2,42 \text{ kW}$$

$$P_R = \frac{U^2}{R} = 2,42 \text{ kW}$$

$$P_T = P_{L20} + P_H + P_R = 11,62 \text{ kW}$$

$$P_T = 11,62 \text{ kW}$$

$$\varphi_T = \varphi_{L20} + \varphi_H + \varphi_R = \varphi_H$$

2 pts

$$\varphi_H = ? \quad P_H = UI \cos \varphi \quad UI = \frac{P}{\cos \varphi}$$

$$\varphi_T = 3,10^{\circ} \text{ VAR}$$

$$\varphi_H = UI \sin \varphi \quad \sin \varphi = 0,61$$

$$\varphi_H = \frac{P \sin \varphi}{UI} = 3,10^{\circ} \text{ VAR}$$

b)

$$P_T = UI_T \cos \varphi_T$$

$$\tan \varphi = \frac{\varphi_T}{P_T} = \frac{3}{11,62} = 0,258$$

$$\varphi_T = UI \sin \varphi_T$$

$$\varphi = 14,47^{\circ}$$

$$\cos \varphi_T = 0,96 \quad \text{Power factor}$$

$$c) I_T = ? \quad P_T = UI_T \cos \varphi \quad \frac{I_T}{I} = \frac{P_T}{UI \cos \varphi_T} = 110 \text{ A}$$

$$I_T = 110 \text{ A} \quad 1 \text{ pt}$$

EY02 (8pts)

$R = ?$ ,  $B_p = ?$

$$S = 4 \times 5 = 20 \text{ cm}^2 = 0,002 \text{ m}^2$$

1 pt

$$l_{mag} = (20 - 5 + 25 - 5) 2 = 40 \text{ cm} = 0,7 \text{ m}$$

1 pt

$$R_H = \frac{l_{mag}}{\mu_0 \mu_r S} = \frac{0,7}{4 \cdot 10^{-7} \pi \cdot 2100 \times 2 \cdot 10^{-3}} = 111400 \text{ At/m}$$

$$R_H \approx 111400 \text{ At/m}$$

1


$$R_o = \frac{e}{\mu_r S} = \frac{0,5 \times 10^{-2}}{4 \cdot 10^{-7} \pi \cdot 210^{-3}} = 1989436,7 \text{ At/Wb}$$

1

$$R_T = R_H + R_o = 2100836,78 \text{ At/Wb}$$

$$\phi = \frac{NI}{R_T} = 0,238 \times 10^{-3} \text{ wb}$$

1 pts

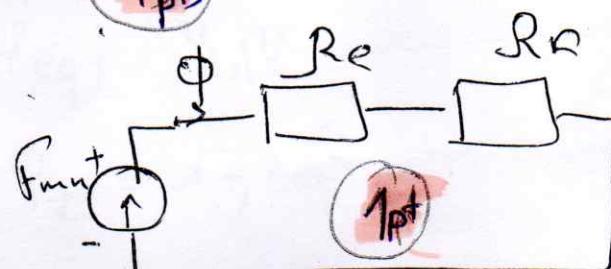

b)  
Y/Y6 transformateur  
abansseur

1  
Primaire  
hautetension  
s/couplage en étoile  
 $6 \times 30^\circ = 180^\circ$

Secondaire Y  
Basse tension  
couplage en étoile  
Indice horaire (decalage  
secondaire primaire)

Dy : 5

D  
Primaire  
hautetension  
couplage en triangle

Secondaire  
Basse tension  
couplage en étoile

EXO 3 (6 pts)

$$1) V = 220\sqrt{2} \sin 314t$$

$$Z_1 = 8 + j10\Omega$$

$$Z_2 = 7 + 9j$$

$$Z_3 = 5 - 2j$$

$$2) Z_{eq} = (Z_1 \parallel Z_2) \text{ en Sén avec } Z_3$$

$$\begin{aligned} Z_{eq} &= \frac{Z_1 Z_2}{Z_1 + Z_2} + Z_3 = \frac{(8 + j10)(7 + 9j)}{15 + 19j} + \frac{(15 - 19j)}{(15 - 19j)} + 5 - 2j \\ &= \frac{2,188 + 277,6j}{225 + 361} + 5 - 2j = 8,73 + 2,73j \end{aligned}$$

$$Z_{eq} = 8,73 + j2,73$$

$$|I| = \frac{V}{Z_{eq}} = 24 \text{ A}$$

$$\varphi_z = 17,36^\circ$$

$$|Z_{eq}| = 9,14$$

$$\varphi_I = -\varphi_z = -17,36^\circ \quad \varphi_z = 17,36^\circ$$

$$i(t) = 24\sqrt{2} \sin(314t - 17,36^\circ)$$

$$I = 24 e^{-j17,36}$$

$$3) Z = 8,73 + j2,73$$

La partie réelle est positive  
la partie imaginaire est > 0